Complete cabeling/circuit **IMPORTANT !!!** J? SOLIS COM You need to shorten this two points JST Capacitor 1000µf 1N ▼.58 17 HV4 HV3 GND HV HV2 HV1 Level Converter LV4 LV3 CND LV LV2 LVI 33k 47k

Building the circuit board



